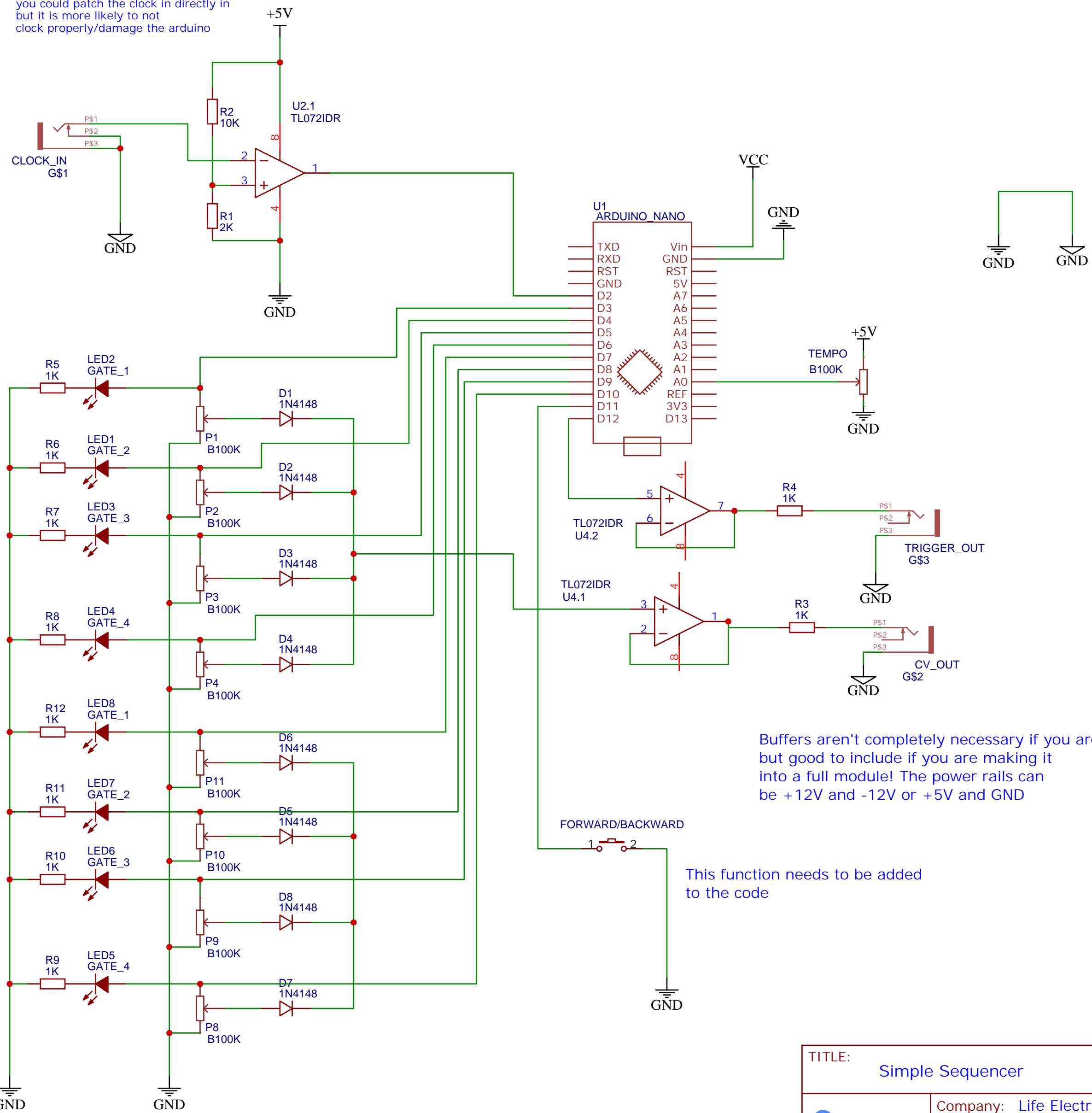


The comparator here is not essential;  
you could patch the clock in directly in  
but it is more likely to not  
clock properly/damage the arduino



Buffers aren't completely necessary if you are prototyping  
but good to include if you are making it  
into a full module! The power rails can  
be +12V and -12V or +5V and GND

This function needs to be added  
to the code

TITLE: Simple Sequencer		REV: 1.0
EasyEDA	Company: Life Electric	Sheet: 1/1
	Date: 2020-10-27	Drawn By: freddie.renyard